

INDIVIDUAL ASSIGNMENT

Number System, Digital Logic and Boolean Algebra



Dr. KUNDAN Kumar
LECTURER

June 2025

Table of Contents

QUESTION 1: BINARY SUBTRACTION AND 2'S COMPLEMENT CONCEPT	2
QUESTION 2: LOGIC GATE IMPLEMENTATION USING UNIVERSAL GATES	2
QUESTION 3: BOOLEAN ALGEBRA – SIMPLIFYING EXPRESSIONS.....	3
ASSIGNMENT REPORT GUIDELINES – HYBRID FORMAT	3
SUBMISSION DEADLINE	4

QUESTION 1: BINARY SUBTRACTION AND 2'S COMPLEMENT CONCEPT

- a) Explain why 2's complement is essential in binary subtraction involving signed numbers. Provide an example using 4-bit binary numbers to illustrate subtraction of a larger number from a smaller one.

For example: $A = 0100_2$ and $B = 1011_2$, what happens If you try to subtract 1101_2 from 0101_2 using basic binary subtraction rules, what problem will they face? Demonstrate the solution using 2's complement.

QUESTION 2: LOGIC GATE IMPLEMENTATION USING UNIVERSAL GATES

- a) Design an AND gate using only NAND gates. Show your implementation with a truth table and circuit diagram.
- b) Design an OR gate using only NAND gates. Show your implementation with a truth table and circuit diagram.
- c) Design a NOT gate using only NAND gate. Show your implementation with a truth table and circuit diagram.
- d) 4) Design an AND gate using only NOR gates. Show your implementation with a truth table and circuit diagram.
- e) 5) Design an OR gate using only NOR gates. Show your implementation with a truth table and circuit diagram.
- f) Design a NOT gate using only NOR gate. Show your implementation with a truth table and circuit diagram.

N.B.

- Don't forget to test your implemented circuits using the **Logic.ly Simulator (visit this link to use this simulator <https://logic.ly/demo/>)**
- For guidance, Lecturer have shared a demo own video on how to use this simulator: <https://youtu.be/Wge0APXzkqE>

- Please take a **screenshot** of your tested circuit and **attach it to your assignment report**.

QUESTION 3: BOOLEAN ALGEBRA – SIMPLIFYING EXPRESSIONS

A revision video on Boolean Algebra, recorded by the lecturer, has been provided to support your learning. Watch here: https://youtu.be/j_oZOIOV_tg

- a) $AB + A\bar{B} + \bar{A}B$
- b) $(A + B)(A + \bar{B})(\bar{A} + B)$
- c) $\overline{A + BC} + A\bar{B}$
- d) $AB + A\bar{B} + \bar{A}B + \bar{A}\bar{B}$
- e) $\overline{(A + \bar{B}) + (\bar{C} \cdot D)}$
- f) $\overline{A + B \cdot \bar{C}} + D$
- g) $\overline{(A \cdot (\bar{B} + C) + \bar{D} + E)}$
- h) $\overline{(\bar{A} + B) \cdot (C + \bar{D}) + \bar{E}}$

ASSIGNMENT REPORT GUIDELINES – HYBRID FORMAT

a. Handwritten Work

- i. Neatly solve all Number System and Boolean Algebra questions on paper.

b. Digital Circuit Designs

- i. Use the Logicly Simulator <https://logic.ly/demo/> to design the required logic gates.
- ii. Take clear screenshots of your circuit diagrams.
- iii. Paste the screenshots into a Word document, then print and include it with your hard copy submission.

Note: Please compile all pages into a single, well-organized report and ensure they are neatly stapled together in the correct order before submission.

SUBMISSION DEADLINE

- 10th July 2025

===== **Good Luck** =====